

# Contents

## 1 Mealy and Moore m/cs



# Section outline

## 1 Mealy and Moore m/cs

- Mealy m/c
- D flip flop
- Mealy m/c ex 1
- Mealy m/c ex 2
- Mealy m/c ex 3
- Mealy m/c ex 4
- Moore m/c
- Moore m/c ex 1
- Moore m/c ex 2
- Moore m/c ex 3
- Moore m/c ex 4
- Mealy to Moore conversion
- Mealy→Moore ex 1
- Mealy→Moore ex 2
- Moore→Mealy ex 1




# Mealy m/c

- Mealy machines are finite state machines whose outputs depends on the present state and on the inputs
- It can be defined as  $\langle Q, q_0, \Sigma, \Delta, \delta, \lambda \rangle$  where:
  - $Q$  is a finite set of states
  - $q_0$  is the initial state
  - $\Sigma$  is the input alphabet
  - $\Delta$  is the output alphabet
  - $\delta$  is transition function which maps  $Q \times \Sigma \rightarrow Q$
  - $\lambda$  is the output function which maps  $Q \times \Sigma \rightarrow \Delta$



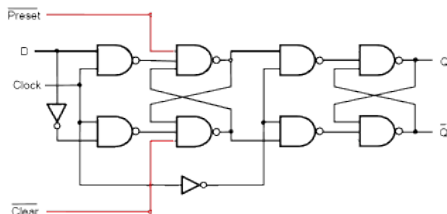
# D flip flop

- At the appropriate edge of clock data is transferred from D to Q
- Two SR latches in series clocked with complementary clocks to prevent racing through the FF and the combinational circuits
- Synchronous or asynchronous preset/clear possible
- Some problems still possible, better circuit to be discussed later



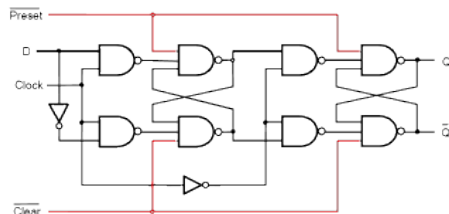DFF (-ve edge) with synchronous present/clear



DFF (-ve edge) with asynchronous present/clear



# Mealy m/c ex 1

## Example (2's complement of input, starting from LSB)


- $\Sigma = \{0, 1\}$
- $\Delta = \{0, 1\}$



# Mealy m/c ex 1
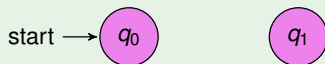
## Example (2's complement of input, starting from LSB)


- $\Sigma = \{0, 1\}$
- $\Delta = \{0, 1\}$



# Mealy m/c ex 1
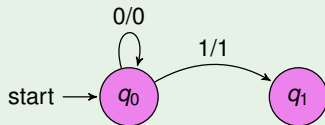
## Example (2's complement of input, starting from LSB)


- $\Sigma = \{0, 1\}$
- $\Delta = \{0, 1\}$



# Mealy m/c ex 1
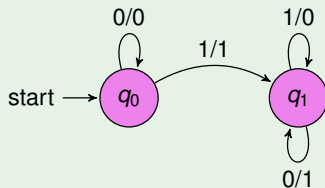
## Example (2's complement of input, starting from LSB)

- $\Sigma = \{0, 1\}$
- $\Delta = \{0, 1\}$






# Mealy m/c ex 1
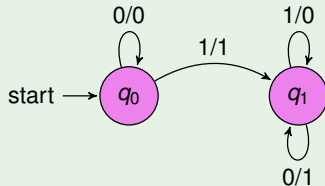
## Example (2's complement of input, starting from LSB)

- $\Sigma = \{0, 1\}$
- $\Delta = \{0, 1\}$




I	0		1	
PS	NS	O	NS	O



# Mealy m/c ex 1
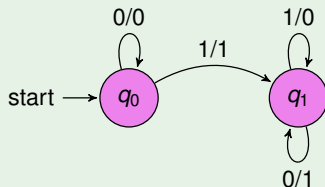
## Example (2's complement of input, starting from LSB)

- $\Sigma = \{0, 1\}$
- $\Delta = \{0, 1\}$




I	0		1	
PS	NS	O	NS	O
$q_0$	$q_0$	0	$q_1$	1



# Mealy m/c ex 1
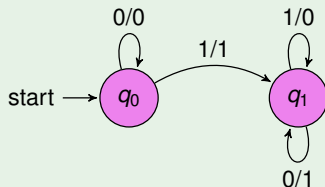
## Example (2's complement of input, starting from LSB)

- $\Sigma = \{0, 1\}$
- $\Delta = \{0, 1\}$




I	0		1	
PS	NS	O	NS	O
$q_0$	$q_0$	0	$q_1$	1
$q_1$	$q_1$	1	$q_0$	0



# Mealy m/c ex 1
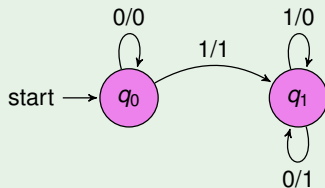
## Example (2's complement of input, starting from LSB)

- $\Sigma = \{0, 1\}$
- $\Delta = \{0, 1\}$



I	0		1	
PS	NS	O	NS	O
$q_0$	$q_0$	0	$q_1$	1
$q_1$	$q_1$	1	$q_1$	0

Encodings

$q_0$	1	$q_1$	0
-------	---	-------	---


Other en-  
codings also  
possible



# Mealy m/c ex 1
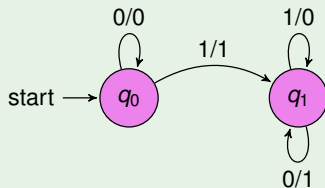
## Example (2's complement of input, starting from LSB)

- $\Sigma = \{0, 1\}$
- $\Delta = \{0, 1\}$



Encodings

$q_0$	1	$q_1$	0
-------	---	-------	---

Other en-  
codings also  
possible

I	0		1	
PS	NS	O	NS	O
$q_0$	$q_0$	0	$q_1$	1
$q_1$	$q_1$	1	$q_1$	0

I	0		1	
PS	NS	O	NS	O
0	0	1	0	0
1	1	0	0	1

Complete the realisation using DFF



# Mealy m/c ex 2


## Example (Output A on 101, B on 110, C otherwise)

- $\Sigma = \{0, 1\}$
- $\Delta = \{A, B, C\}$

## Mealy m/c ex 2

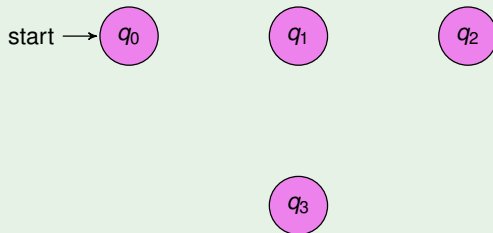Example (Output A on 101, B on 110, C otherwise)


- $\Sigma = \{0, 1\}$
- $\Delta = \{A, B, C\}$



# Mealy m/c ex 2

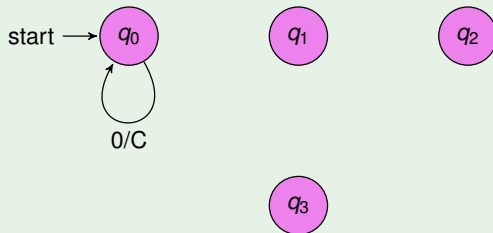Example (Output A on 101, B on 110, C otherwise)

- $\Sigma = \{0, 1\}$
- $\Delta = \{A, B, C\}$






# Mealy m/c ex 2

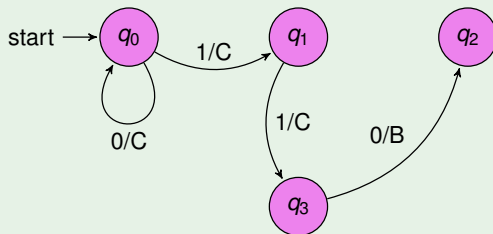Example (Output A on 101, B on 110, C otherwise)


- $\Sigma = \{0, 1\}$
- $\Delta = \{A, B, C\}$



# Mealy m/c ex 2

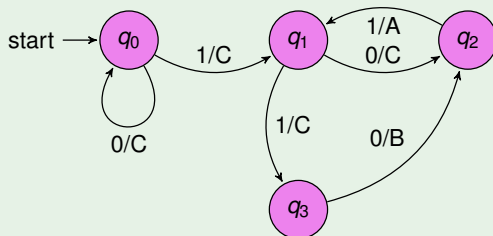Example (Output A on 101, B on 110, C otherwise)


- $\Sigma = \{0, 1\}$
- $\Delta = \{A, B, C\}$



## Mealy m/c ex 2

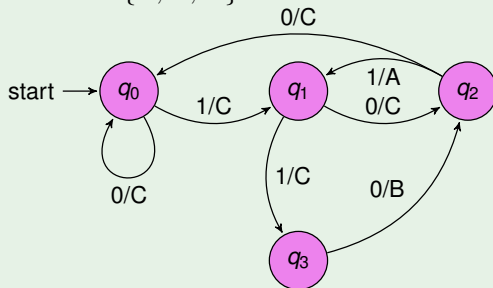Example (Output A on 101, B on 110, C otherwise)


- $\Sigma = \{0, 1\}$
- $\Delta = \{A, B, C\}$



# Mealy m/c ex 2

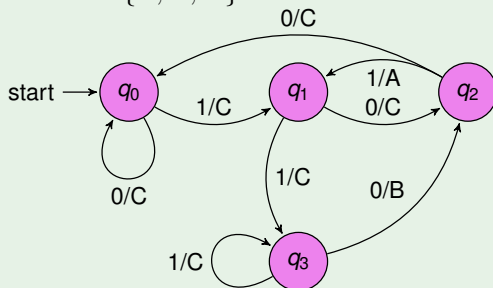Example (Output A on 101, B on 110, C otherwise)


- $\Sigma = \{0, 1\}$
- $\Delta = \{A, B, C\}$



# Mealy m/c ex 2

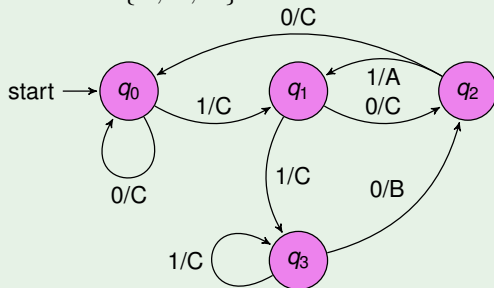Example (Output A on 101, B on 110, C otherwise)

- $\Sigma = \{0, 1\}$
- $\Delta = \{A, B, C\}$




I	0		1	
PS	NS	O	NS	O

# Mealy m/c ex 2

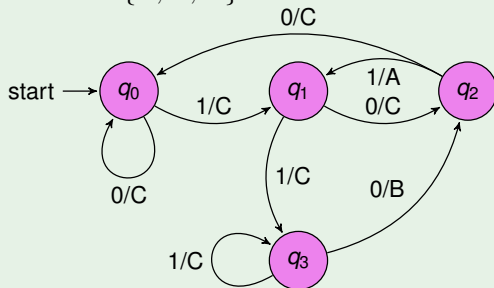Example (Output A on 101, B on 110, C otherwise)

- $\Sigma = \{0, 1\}$
- $\Delta = \{A, B, C\}$




I	0		1	
PS	NS	O	NS	O
$q_0$	$q_0$	C	$q_1$	C

# Mealy m/c ex 2

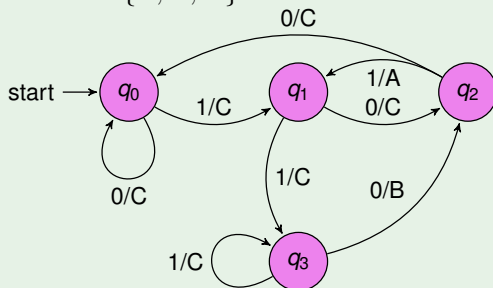Example (Output A on 101, B on 110, C otherwise)

- $\Sigma = \{0, 1\}$
- $\Delta = \{A, B, C\}$




I	0		1	
PS	NS	O	NS	O
$q_0$	$q_0$	C	$q_1$	C
$q_1$	$q_2$	C	$q_3$	C

# Mealy m/c ex 2

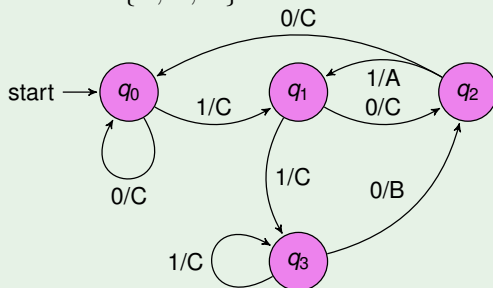Example (Output A on 101, B on 110, C otherwise)

- $\Sigma = \{0, 1\}$
- $\Delta = \{A, B, C\}$




I	0		1	
PS	NS	O	NS	O
$q_0$	$q_0$	C	$q_1$	C
$q_1$	$q_2$	C	$q_3$	C
$q_2$	$q_1$	C	$q_1$	A



# Mealy m/c ex 2

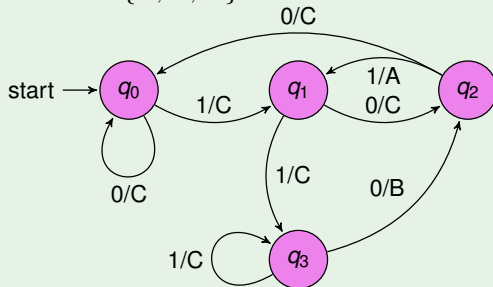Example (Output A on 101, B on 110, C otherwise)

- $\Sigma = \{0, 1\}$
- $\Delta = \{A, B, C\}$




I	0		1	
PS	NS	O	NS	O
$q_0$	$q_0$	C	$q_1$	C
$q_1$	$q_2$	C	$q_3$	C
$q_2$	$q_1$	C	$q_1$	A
$q_3$	$q_2$	B	$q_3$	C

# Mealy m/c ex 2
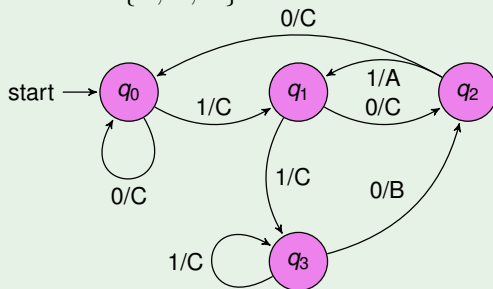
## Example (Output A on 101, B on 110, C otherwise)

- $\Sigma = \{0, 1\}$
- $\Delta = \{A, B, C\}$



I	0		1	
	NS	O	NS	O
$q_0$	$q_0$	C	$q_1$	C
$q_1$	$q_2$	C	$q_3$	C
$q_2$	$q_1$	C	$q_1$	A
$q_3$	$q_2$	B	$q_3$	C


### Encodings

$q_0$	00	A	01	Other encodings also possible
$q_1$	01	B	10	
$q_2$	10	C	00	
$q_3$	11			

# Mealy m/c ex 2
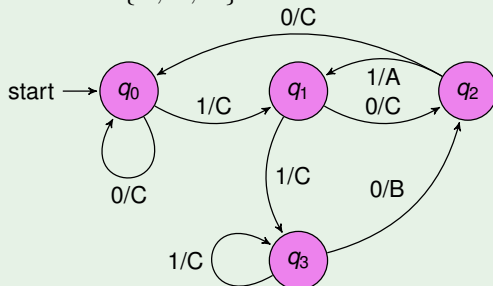
## Example (Output A on 101, B on 110, C otherwise)

- $\Sigma = \{0, 1\}$
- $\Delta = \{A, B, C\}$



### Encodings

$q_0$	00	A	01	Other en-
$q_1$	01	B	10	codings also
$q_2$	10	C	00	possible
$q_3$	11			

I	0		1	
PS	NS	O	NS	O
$q_0$	$q_0$	C	$q_1$	C
$q_1$	$q_2$	C	$q_3$	C
$q_2$	$q_1$	C	$q_1$	A
$q_3$	$q_2$	B	$q_3$	C

I	0		1	
PS	NS	O	NS	O
00	00	00	01	00
01	10	00	11	00
10	01	00	01	01
11	10	10	11	00

Complete the realisation using DFF

# Mealy m/c ex 3


Example (Output on ending with 00:A, 11:B, C, otherwise)

- $\Sigma = \{0, 1\}$
- $\Delta = \{A, B, C\}$

## Mealy m/c ex 3

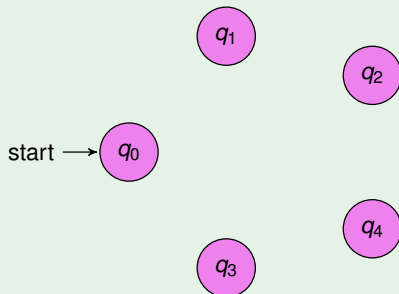Example (Output on ending with 00:A, 11:B, C, otherwise)


- $\Sigma = \{0, 1\}$
- $\Delta = \{A, B, C\}$



# Mealy m/c ex 3

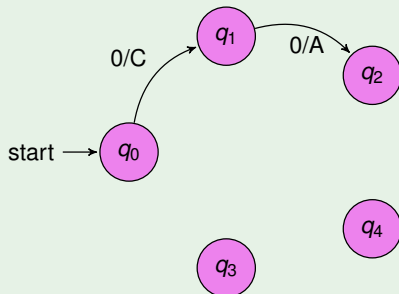Example (Output on ending with 00:A, 11:B, C, otherwise)


- $\Sigma = \{0, 1\}$
- $\Delta = \{A, B, C\}$



# Mealy m/c ex 3

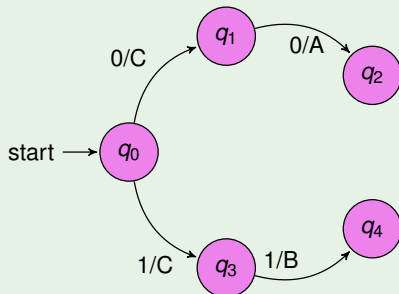Example (Output on ending with 00:A, 11:B, C, otherwise)


- $\Sigma = \{0, 1\}$
- $\Delta = \{A, B, C\}$



# Mealy m/c ex 3

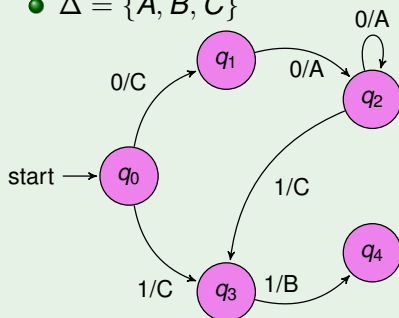Example (Output on ending with 00:A, 11:B, C, otherwise)

- $\Sigma = \{0, 1\}$
- $\Delta = \{A, B, C\}$






# Mealy m/c ex 3

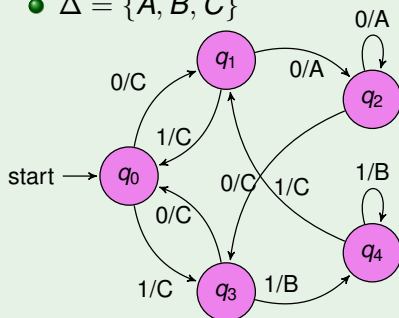Example (Output on ending with 00:A, 11:B, C, otherwise)


- $\Sigma = \{0, 1\}$
- $\Delta = \{A, B, C\}$



# Mealy m/c ex 3

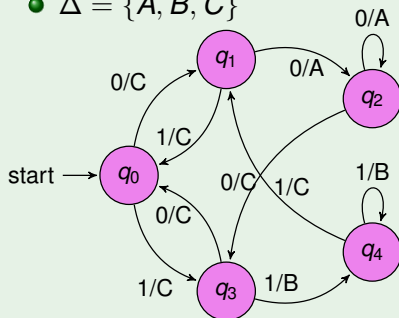Example (Output on ending with 00:A, 11:B, C, otherwise)

- $\Sigma = \{0, 1\}$
- $\Delta = \{A, B, C\}$




I	0		1	
PS	NS	O	NS	O

# Mealy m/c ex 3

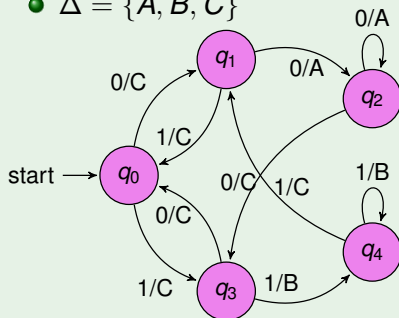Example (Output on ending with 00:A, 11:B, C, otherwise)

- $\Sigma = \{0, 1\}$
- $\Delta = \{A, B, C\}$




I	0		1	
PS	NS	O	NS	O
$q_0$	$q_1$	C	$q_3$	C

# Mealy m/c ex 3

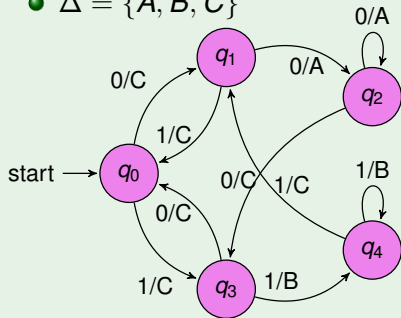Example (Output on ending with 00:A, 11:B, C, otherwise)

- $\Sigma = \{0, 1\}$
- $\Delta = \{A, B, C\}$




I	0		1	
PS	NS	O	NS	O
$q_0$	$q_1$	C	$q_3$	C
$q_1$	$q_2$	A	$q_0$	C

# Mealy m/c ex 3

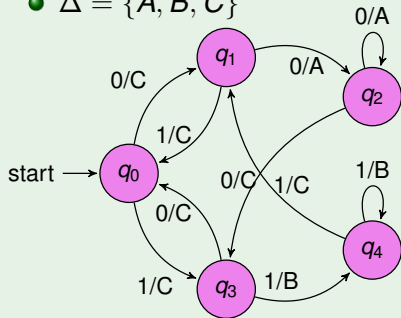Example (Output on ending with 00:A, 11:B, C, otherwise)

- $\Sigma = \{0, 1\}$
- $\Delta = \{A, B, C\}$




I	0		1	
PS	NS	O	NS	O
$q_0$	$q_1$	C	$q_3$	C
$q_1$	$q_2$	A	$q_0$	C
$q_2$	$q_2$	A	$q_3$	C

# Mealy m/c ex 3

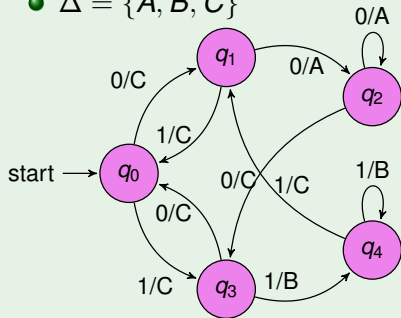Example (Output on ending with 00:A, 11:B, C, otherwise)

- $\Sigma = \{0, 1\}$
- $\Delta = \{A, B, C\}$




I	0		1	
PS	NS	O	NS	O
$q_0$	$q_1$	C	$q_3$	C
$q_1$	$q_2$	A	$q_0$	C
$q_2$	$q_2$	A	$q_3$	C
$q_3$	$q_0$	C	$q_4$	B

# Mealy m/c ex 3

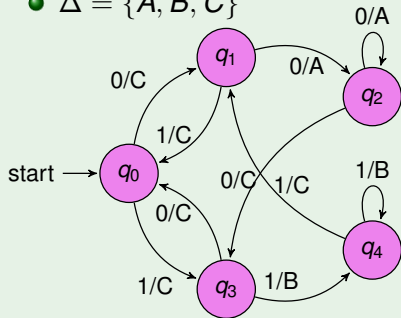Example (Output on ending with 00:A, 11:B, C, otherwise)

- $\Sigma = \{0, 1\}$
- $\Delta = \{A, B, C\}$




I	0		1	
PS	NS	O	NS	O
$q_0$	$q_1$	C	$q_3$	C
$q_1$	$q_2$	A	$q_0$	C
$q_2$	$q_2$	A	$q_3$	C
$q_3$	$q_0$	C	$q_4$	B
$q_4$	$q_1$	C	$q_4$	B

# Mealy m/c ex 3

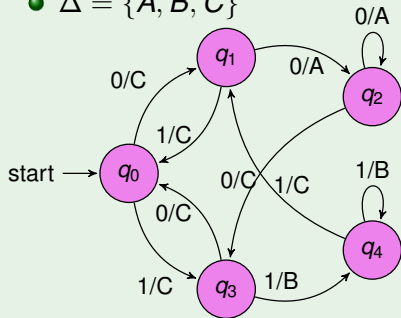Example (Output on ending with 00:A, 11:B, C, otherwise)

- $\Sigma = \{0, 1\}$
- $\Delta = \{A, B, C\}$



Encodings

$q_0$	000	$q_3$	011	A	01
$q_1$	001	$q_4$	100	B	10
$q_2$	010			C	00


I	0		1	
PS	NS	O	NS	O
$q_0$	$q_1$	C	$q_3$	C
$q_1$	$q_2$	A	$q_0$	C
$q_2$	$q_2$	A	$q_3$	C
$q_3$	$q_0$	C	$q_4$	B
$q_4$	$q_1$	C	$q_4$	B



# Mealy m/c ex 3

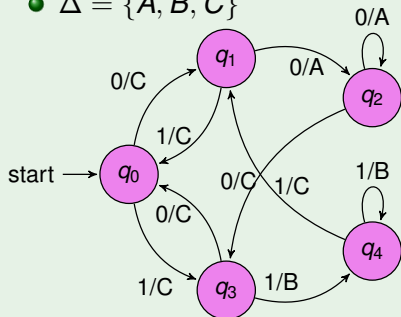Example (Output on ending with 00:A, 11:B, C, otherwise)

- $\Sigma = \{0, 1\}$
- $\Delta = \{A, B, C\}$



Encodings

$q_0$	000	$q_3$	011	A	01
$q_1$	001	$q_4$	100	B	10
$q_2$	010			C	00

I	0		1	
PS	NS	O	NS	O
$q_0$	$q_1$	C	$q_3$	C
$q_1$	$q_2$	A	$q_0$	C
$q_2$	$q_2$	A	$q_3$	C
$q_3$	$q_0$	C	$q_4$	B
$q_4$	$q_1$	C	$q_4$	B

I	0		1	
PS	NS	O	NS	O
000	001	00	011	00
001	010	01	000	00
010	010	01	011	00
010	000	00	100	01
100	001	00	100	01

Complete the realisation using DFF

## Mealy m/c ex 4


### Example (Serial adder, starting from LSB)

- $\Sigma = \{00, 01, 10, 11\} \triangleq \{\langle a_i, b_i \rangle\}, i \geq 0$
- $\Delta = \{00, 01, 10, 11\} \triangleq \{\langle s_i, c_i^0 \rangle\}, i \geq 0$

# Mealy m/c ex 4
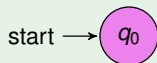
## Example (Serial adder, starting from LSB)


- $\Sigma = \{00, 01, 10, 11\} \triangleq \{\langle a_i, b_i \rangle\}, i \geq 0$
- $\Delta = \{00, 01, 10, 11\} \triangleq \{\langle s_i, c_i^0 \rangle\}, i \geq 0$



# Mealy m/c ex 4
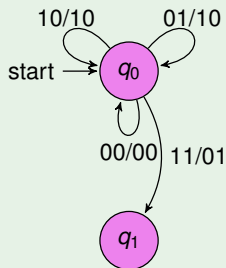
## Example (Serial adder, starting from LSB)


- $\Sigma = \{00, 01, 10, 11\} \triangleq \{\langle a_i, b_i \rangle\}, i \geq 0$
- $\Delta = \{00, 01, 10, 11\} \triangleq \{\langle s_i, c_i^0 \rangle\}, i \geq 0$



# Mealy m/c ex 4
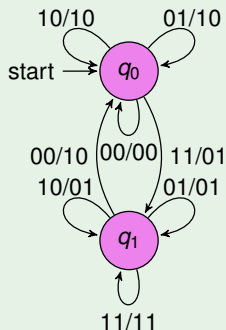
## Example (Serial adder, starting from LSB)


- $\Sigma = \{00, 01, 10, 11\} \triangleq \{\langle a_i, b_i \rangle\}, i \geq 0$
- $\Delta = \{00, 01, 10, 11\} \triangleq \{\langle s_i, c_i^0 \rangle\}, i \geq 0$



# Mealy m/c ex 4
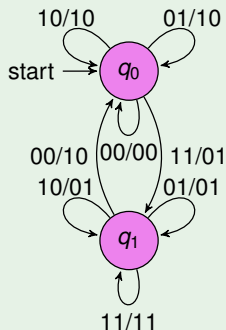
## Example (Serial adder, starting from LSB)

- $\Sigma = \{00, 01, 10, 11\} \triangleq \{\langle a_i, b_i \rangle\}, i \geq 0$
- $\Delta = \{00, 01, 10, 11\} \triangleq \{\langle s_i, c_i^0 \rangle\}, i \geq 0$




I	00		01		10		11	
PS	NS	O	NS	O	NS	O	NS	O

# Mealy m/c ex 4
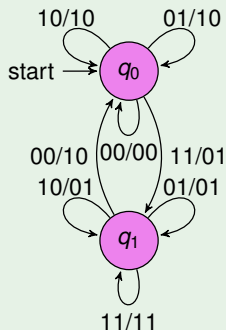
## Example (Serial adder, starting from LSB)

- $\Sigma = \{00, 01, 10, 11\} \triangleq \{\langle a_i, b_i \rangle\}, i \geq 0$
- $\Delta = \{00, 01, 10, 11\} \triangleq \{\langle s_i, c_i^0 \rangle\}, i \geq 0$




I	00		01		10		11	
PS	NS	O	NS	O	NS	O	NS	O
$q_0$	$q_0$	00	$q_0$	10	$q_0$	10	$q_1$	01

# Mealy m/c ex 4
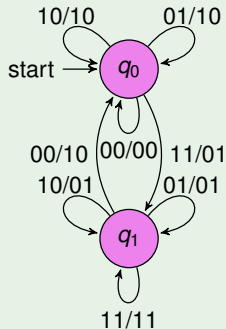
## Example (Serial adder, starting from LSB)

- $\Sigma = \{00, 01, 10, 11\} \triangleq \{\langle a_i, b_i \rangle\}, i \geq 0$
- $\Delta = \{00, 01, 10, 11\} \triangleq \{\langle s_i, c_i^0 \rangle\}, i \geq 0$




I	00		01		10		11	
PS	NS	O	NS	O	NS	O	NS	O
$q_0$	$q_0$	00	$q_0$	10	$q_0$	10	$q_1$	01
$q_1$	$q_0$	10	$q_1$	01	$q_1$	01	$q_1$	11



# Mealy m/c ex 4
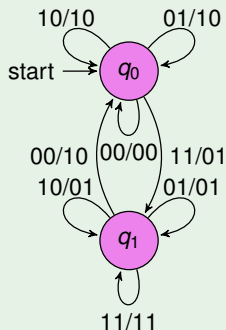
## Example (Serial adder, starting from LSB)

- $\Sigma = \{00, 01, 10, 11\} \triangleq \{\langle a_i, b_i \rangle\}, i \geq 0$
- $\Delta = \{00, 01, 10, 11\} \triangleq \{\langle s_i, c_i^0 \rangle\}, i \geq 0$



I	00		01		10		11	
PS	NS	O	NS	O	NS	O	NS	O
$q_0$	$q_0$	00	$q_0$	10	$q_0$	10	$q_1$	01
$q_1$	$q_0$	10	$q_1$	01	$q_1$	01	$q_1$	11


Encodings

$q_0$	0	$q_1$	1
-------	---	-------	---

# Mealy m/c ex 4
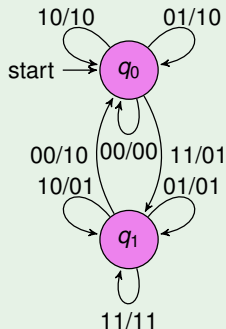
## Example (Serial adder, starting from LSB)

- $\Sigma = \{00, 01, 10, 11\} \triangleq \{\langle a_i, b_i \rangle\}, i \geq 0$
- $\Delta = \{00, 01, 10, 11\} \triangleq \{\langle s_i, c_i^0 \rangle\}, i \geq 0$



Encodings

$q_0$	0	$q_1$	1
-------	---	-------	---

I	00		01		10		11	
PS	NS	O	NS	O	NS	O	NS	O
$q_0$	$q_0$	00	$q_0$	10	$q_0$	10	$q_1$	01
$q_1$	$q_0$	10	$q_1$	01	$q_1$	01	$q_1$	11

I	00		01		10		11	
PS	NS	O	NS	O	NS	O	NS	O
0	0	00	0	10	0	10	1	01
1	0	10	1	01	1	01	1	11

Complete the realisation using DFF

# Moore m/c

- Moore machines are finite state machines whose outputs depends only on the present state
- It can be defined as  $\langle Q, q_0, \Sigma, \Delta, \delta, \lambda \rangle$  where:
  - $Q$  is a finite set of states
  - $q_0$  is the initial state
  - $\Sigma$  is the input alphabet
  - $\Delta$  is the output alphabet
  - $\delta$  is transition function which maps  $Q \times \Sigma \rightarrow Q$
  - $\lambda$  is the output function which maps  $Q \rightarrow \Delta$



# Moore m/c

- Moore machines are finite state machines whose outputs depends only on the present state
- It can be defined as  $\langle Q, q_0, \Sigma, \Delta, \delta, \lambda \rangle$  where:
  - $Q$  is a finite set of states
  - $q_0$  is the initial state
  - $\Sigma$  is the input alphabet
  - $\Delta$  is the output alphabet
  - $\delta$  is transition function which maps  $Q \times \Sigma \rightarrow Q$
  - $\lambda$  is the output function which maps  $Q \rightarrow \Delta$

## Conversion of Moore m/c to a Mealy m/c


- The Mealy m/c has the same set of states and transitions as the Moore m/c
- $\forall a \in \Sigma, q \in Q : \lambda_{\text{Mealy}}(q, a) = \lambda_{\text{Moore}}(\delta_{\text{Moore}}(q, a))$



# Moore m/c ex 1
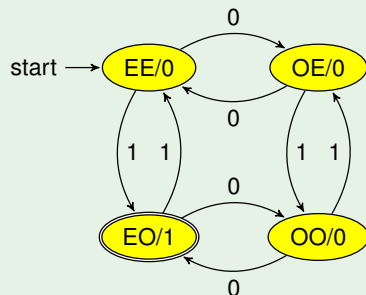
## Example (Acceptor for even 0s, odd 1s)

- $\Sigma = \{0, 1\}$
- $\Delta = \{0, 1\}$




### Encodings

EE	00	OE	01
EO	01	OO	11

# Moore m/c ex 1
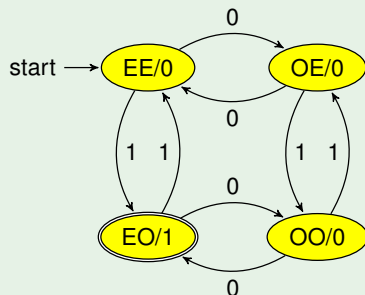
## Example (Acceptor for even 0s, odd 1s)

- $\Sigma = \{0, 1\}$
- $\Delta = \{0, 1\}$



PS	NS		O
	I=0	I=1	
EE	OE	EO	0
OE	EE	OO	0
EO	OO	EE	1
OO	EO	OE	0


### Encodings

EE	00	OE	01
EO	01	OO	11

# Moore m/c ex 1
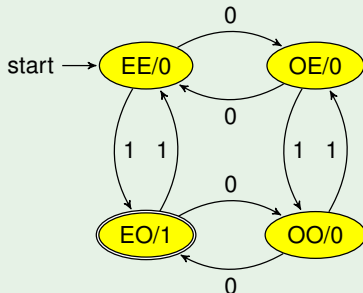
## Example (Acceptor for even 0s, odd 1s)

- $\Sigma = \{0, 1\}$
- $\Delta = \{0, 1\}$



Encodings

EE	00	OE	01
EO	01	OO	11

PS	NS		O
	I=0	I=1	
EE	OE	EO	0
OE	EE	OO	0
EO	OO	EE	1
OO	EO	OE	0

PS	NS		O
	I=0	I=1	
00	10	10	0
10	00	11	0
10	11	00	1
11	10	10	0

Complete the realisation using DFF

# Moore m/c ex 2

## Example (Remainder on division by 3, from MSB)

- $\Sigma = \{0, 1\}$
- $\Delta = \{00, 01, 10\}$

Encodings

R0	00	R1	01	R2	10
----	----	----	----	----	----

- Initial remainder is taken as zero
- On every new bit existing remainder is doubled
- Also, add 1 to new remainder on getting 1, nothing for 0






# Moore m/c ex 2
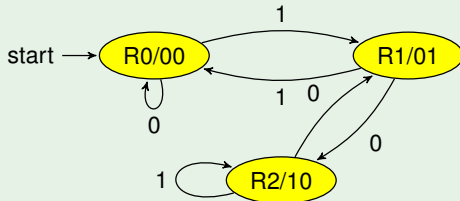
## Example (Remainder on division by 3, from MSB)

- $\Sigma = \{0, 1\}$
- $\Delta = \{00, 01, 10\}$



Encodings

R0	00	R1	01	R2	10
----	----	----	----	----	----


- Initial remainder is taken as zero
- On every new bit existing remainder is doubled
- Also, add 1 to new remainder on getting 1, nothing for 0



# Moore m/c ex 2
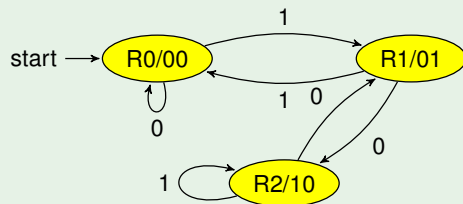
## Example (Remainder on division by 3, from MSB)

- $\Sigma = \{0, 1\}$
- $\Delta = \{00, 01, 10\}$



Encodings

R0	00	R1	01	R2	10
----	----	----	----	----	----

- Initial remainder is taken as zero
- On every new bit existing remainder is doubled
- Also, add 1 to new remainder on getting 1, nothing for 0

PS	NS		O
	I=0	I=1	
R0 (00)	R0 (00)	R1 (01)	00
R1 (01)	R2 (10)	R0 (00)	01
R2 (10)	R1 (01)	R2 (10)	10

Complete the realisation using DFF



## Moore m/c ex 3


### Example (Remainder on division by 3, from LSB)

- $\Sigma = \{0, 1\}$
- $\Delta = \{00, 01, 10\}$
- Initial remainder is taken as zero
- 1 on an even index bit adds 1 to the accumulated remainder
- 1 on an odd index bit adds 2 to the accumulated remainder
- Need to keep track of parity of bit index being handled

# Moore m/c ex 3
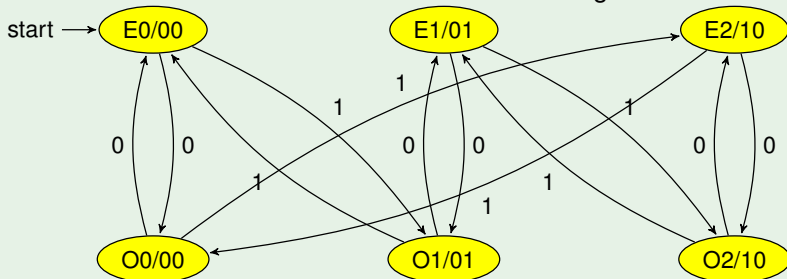
## Example (Remainder on division by 3, from LSB)

- $\Sigma = \{0, 1\}$
- $\Delta = \{00, 01, 10\}$
- Initial remainder is taken as zero
- 1 on an even index bit adds 1 to the accumulated remainder
- 1 on an odd index bit adds 2 to the accumulated remainder
- Need to keep track of parity of bit index being handled



# Moore m/c ex 3

## Example (Remainder on division by 3, from LSB)


- $\Sigma = \{0, 1\}$
- $\Delta = \{00, 01, 10\}$

Encodings

E0	000	E1	001	E2	010
O0	100	O1	101	O2	110

- Initial remainder is taken as zero
- 1 on an even index bit adds 1 to the accumulated remainder
- 1 on an odd index bit adds 2 to the accumulated remainder
- Need to keep track of parity of bit index being handled


Complete the realisation using DFF

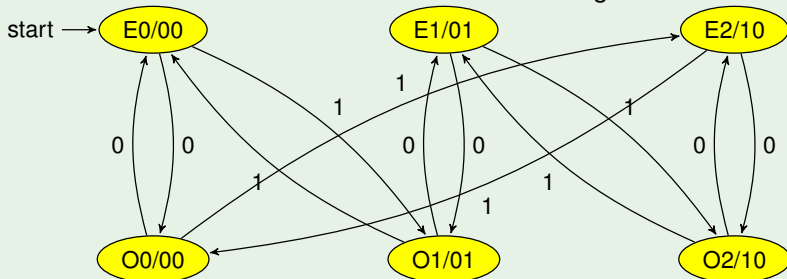

## Moore m/c ex 4

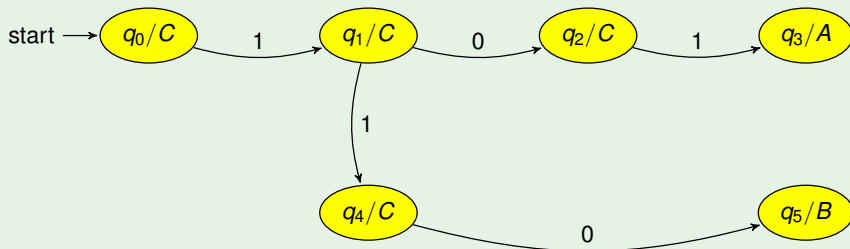Example (Output A on 101, B on 110, C otherwise)


- $\Sigma = \{0, 1\}$
- $\Delta = \{00, 01, 10\} \triangleq \{C, A, B\}$



## Moore m/c ex 4

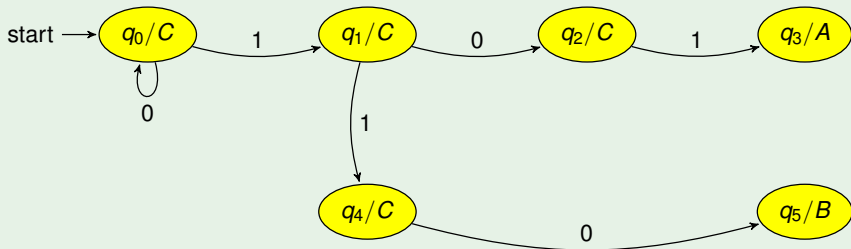Example (Output A on 101, B on 110, C otherwise)


- $\Sigma = \{0, 1\}$
- $\Delta = \{00, 01, 10\} \triangleq \{C, A, B\}$



## Moore m/c ex 4

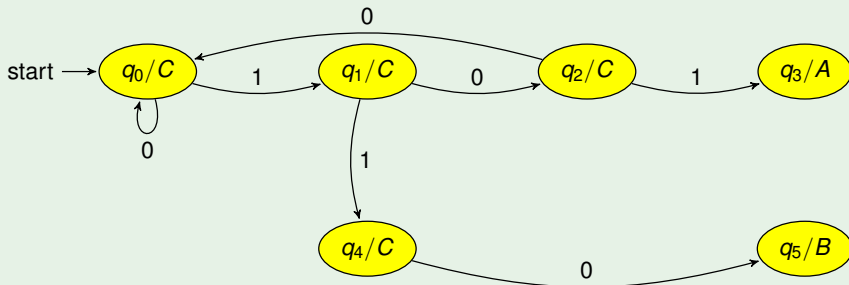Example (Output A on 101, B on 110, C otherwise)

- $\Sigma = \{0, 1\}$
- $\Delta = \{00, 01, 10\} \triangleq \{C, A, B\}$






## Moore m/c ex 4

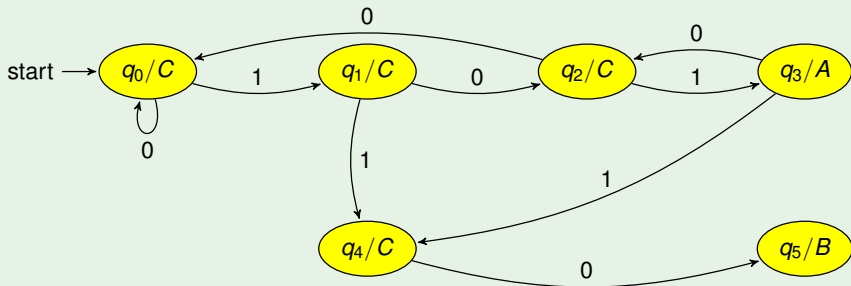Example (Output A on 101, B on 110, C otherwise)


- $\Sigma = \{0, 1\}$
- $\Delta = \{00, 01, 10\} \triangleq \{C, A, B\}$



## Moore m/c ex 4

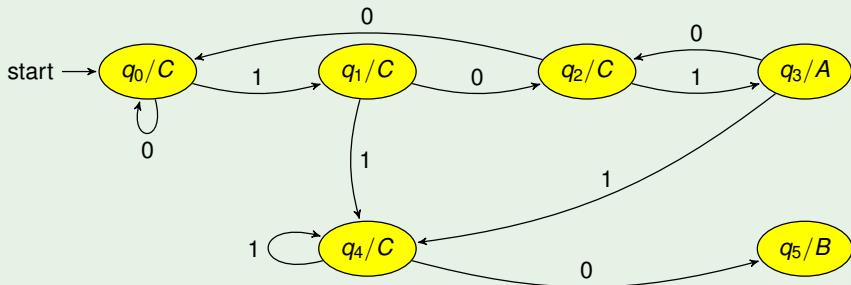Example (Output A on 101, B on 110, C otherwise)


- $\Sigma = \{0, 1\}$
- $\Delta = \{00, 01, 10\} \triangleq \{C, A, B\}$



## Moore m/c ex 4

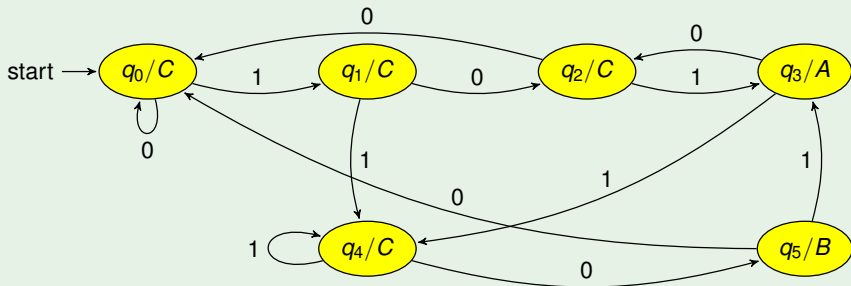Example (Output A on 101, B on 110, C otherwise)

- $\Sigma = \{0, 1\}$
- $\Delta = \{00, 01, 10\} \triangleq \{C, A, B\}$



# Moore m/c ex 4


**Example (Output A on 101, B on 110, C otherwise)**

- $\Sigma = \{0, 1\}$
- $\Delta = \{00, 01, 10\} \triangleq \{C, A, B\}$

Encodings

$q_0$	000	$q_1$	001	$q_2$	011	$A$	01	$C$	00
$q_3$	010	$q_4$	110	$q_5$	111	$B$	10		

Complete the realisation using DFF

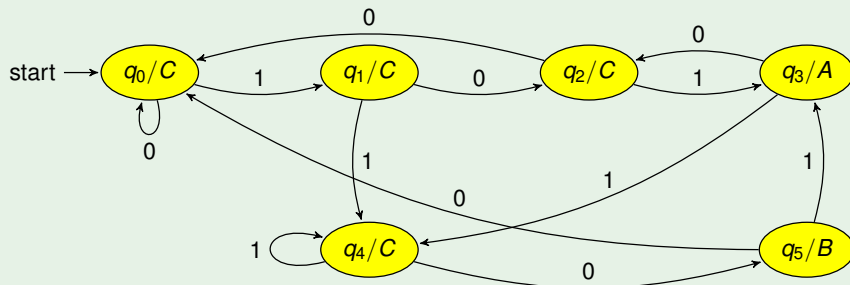

# Mealy to Moore conversion

- In the Mealy m/c let  $s_i$  have input transitions with outputs  $o_{j_1}, o_{j_2}, \dots, o_{j_i}$



# Mealy to Moore conversion

- In the Mealy m/c let  $s_i$  have input transitions with outputs  $o_{j_1}, o_{j_2}, \dots, o_{j_i}$
- In the Moore m/c create states  $s_{i,j_1}/o_{j_1}, s_{i,j_2}/o_{j_2}, \dots, s_{i,j_i}/o_{j_i}$



# Mealy to Moore conversion

- In the Mealy m/c let  $s_i$  have input transitions with outputs  $o_{j_1}, o_{j_2}, \dots, o_{j_i}$
- In the Moore m/c create states  $s_{i,j_1}/o_{j_1}, s_{i,j_2}/o_{j_2}, \dots, s_{i,j_i}/o_{j_i}$
- $s_{i,j_k}/o_{j_k}$  means copy of Mealy m/c state  $s_i$  as  $s_{i,j_k}$  to output  $o_{j_k}$  in the Moore m/c



# Mealy to Moore conversion

- In the Mealy m/c let  $s_i$  have input transitions with outputs  $o_{j_1}, o_{j_2}, \dots, o_{j_i}$
- In the Moore m/c create states  $s_{i,j_1}/o_{j_1}, s_{i,j_2}/o_{j_2}, \dots, s_{i,j_i}/o_{j_i}$
- $s_{i,j_k}/o_{j_k}$  means copy of Mealy m/c state  $s_i$  as  $s_{i,j_k}$  to output  $o_{j_k}$  in the Moore m/c
- If there is a transition from  $s_i$  to  $s_j$  on input  $a$  with output  $o_k$  in the Mealy m/c, create a transition on  $a$  from each copy of  $s_i$  to  $s_{j,k}$





# Mealy to Moore conversion

- In the Mealy m/c let  $s_i$  have input transitions with outputs  $o_{j_1}, o_{j_2}, \dots, o_{j_i}$
- In the Moore m/c create states  $s_{i,j_1}/o_{j_1}, s_{i,j_2}/o_{j_2}, \dots, s_{i,j_i}/o_{j_i}$
- $s_{i,j_k}/o_{j_k}$  means copy of Mealy m/c state  $s_i$  as  $s_{i,j_k}$  to output  $o_{j_k}$  in the Moore m/c
- If there is a transition from  $s_i$  to  $s_j$  on input  $a$  with output  $o_k$  in the Mealy m/c, create a transition on  $a$  from each copy of  $s_i$  to  $s_{j,k}$
- For the Moore m/c, let  $o_\epsilon$  be a special symbol which is output at the beginning when no inputs have been received, then
 
$$\Delta_{\text{Moore}} = \Delta_{\text{Mealy}} \cup \{o_\epsilon\}$$



# Mealy to Moore conversion

- In the Mealy m/c let  $s_i$  have input transitions with outputs  $o_{j_1}, o_{j_2}, \dots, o_{j_i}$
- In the Moore m/c create states  $s_{i,j_1}/o_{j_1}, s_{i,j_2}/o_{j_2}, \dots, s_{i,j_i}/o_{j_i}$
- $s_{i,j_k}/o_{j_k}$  means copy of Mealy m/c state  $s_i$  as  $s_{i,j_k}$  to output  $o_{j_k}$  in the Moore m/c
- If there is a transition from  $s_i$  to  $s_j$  on input  $a$  with output  $o_k$  in the Mealy m/c, create a transition on  $a$  from each copy of  $s_i$  to  $s_{j,k}$
- For the Moore m/c, let  $o_\epsilon$  be a special symbol which is output at the beginning when no inputs have been received, then  

$$\Delta_{\text{Moore}} = \Delta_{\text{Mealy}} \cup \{o_\epsilon\}$$
- A new state  $q'_0/o_\epsilon$  is created as the initial state of the Moore m/c



# Mealy to Moore conversion

- In the Mealy m/c let  $s_i$  have input transitions with outputs  $o_{j_1}, o_{j_2}, \dots, o_{j_i}$
- In the Moore m/c create states  $s_{i,j_1}/o_{j_1}, s_{i,j_2}/o_{j_2}, \dots, s_{i,j_i}/o_{j_i}$
- $s_{i,j_k}/o_{j_k}$  means copy of Mealy m/c state  $s_i$  as  $s_{i,j_k}$  to output  $o_{j_k}$  in the Moore m/c
- If there is a transition from  $s_i$  to  $s_j$  on input  $a$  with output  $o_k$  in the Mealy m/c, create a transition on  $a$  from each copy of  $s_i$  to  $s_{j,k}$
- For the Moore m/c, let  $o_\epsilon$  be a special symbol which is output at the beginning when no inputs have been received, then
 
$$\Delta_{\text{Moore}} = \Delta_{\text{Mealy}} \cup \{o_\epsilon\}$$
- A new state  $q'_0/o_\epsilon$  is created as the initial state of the Moore m/c
- Successors of  $q'_0/o_\epsilon$  are same as those of any copy of  $q_0$  in the created Moore m/c




# Mealy to Moore conversion

- In the Mealy m/c let  $s_i$  have input transitions with outputs  $o_{j_1}, o_{j_2}, \dots, o_{j_i}$
- In the Moore m/c create states  $s_{i,j_1}/o_{j_1}, s_{i,j_2}/o_{j_2}, \dots, s_{i,j_i}/o_{j_i}$
- $s_{i,j_k}/o_{j_k}$  means copy of Mealy m/c state  $s_i$  as  $s_{i,j_k}$  to output  $o_{j_k}$  in the Moore m/c
- If there is a transition from  $s_i$  to  $s_j$  on input  $a$  with output  $o_k$  in the Mealy m/c, create a transition on  $a$  from each copy of  $s_i$  to  $s_{j,k}$
- For the Moore m/c, let  $o_\epsilon$  be a special symbol which is output at the beginning when no inputs have been received, then
 
$$\Delta_{\text{Moore}} = \Delta_{\text{Mealy}} \cup \{o_\epsilon\}$$
- A new state  $q'_0/o_\epsilon$  is created as the initial state of the Moore m/c
- Successors of  $q'_0/o_\epsilon$  are same as those of any copy of  $q_0$  in the created Moore m/c
- However, if the start state in Mealy m/c has not been split to multiple states, that may be retained as the start state of the Moore m/c; here  $o_\epsilon$  is arbitrarily taken as the unique output of  $q_0$





# Mealy $\rightarrow$ Moore ex 1
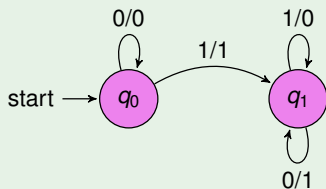
## Example (2's complement of input, starting from LSB)



# Mealy $\rightarrow$ Moore ex 1

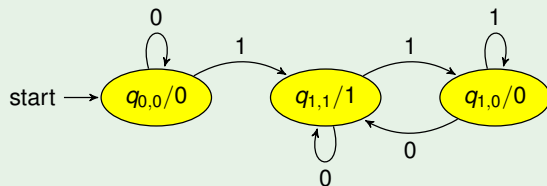
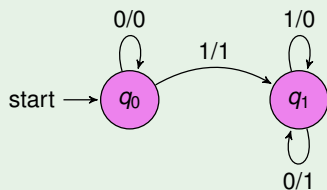
## Example (2's complement of input, starting from LSB)



Here the output initial state state has been set to 0 as all incoming transitions to  $q_0$  in the Mealy m/c had output a 0



# Mealy $\rightarrow$ Moore ex 2
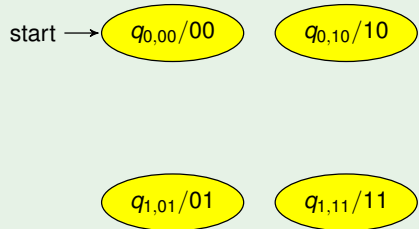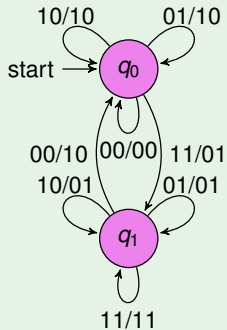
## Example (Serial adder, starting from LSB)



# Mealy $\rightarrow$ Moore ex 2

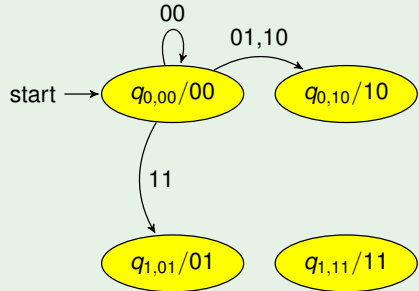
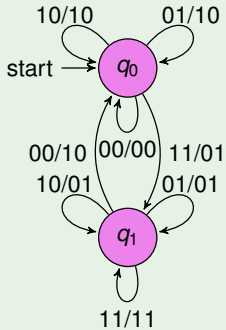
## Example (Serial adder, starting from LSB)







# Mealy → Moore ex 2
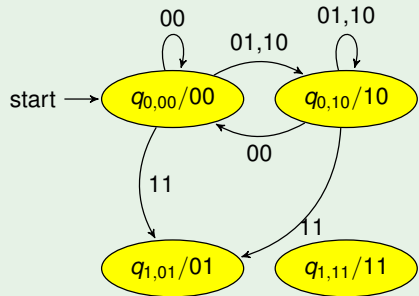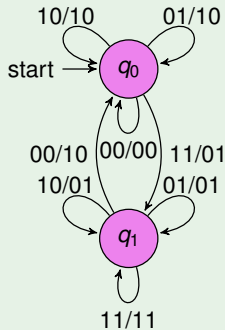
## Example (Serial adder, starting from LSB)





# Mealy → Moore ex 2
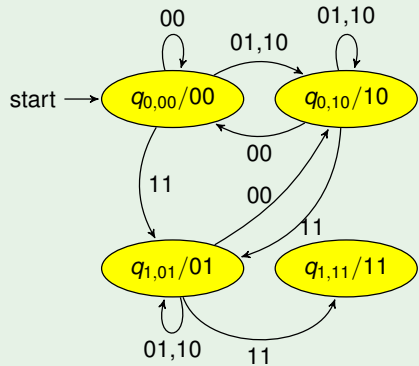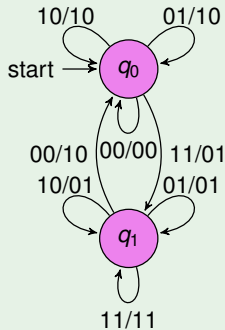
## Example (Serial adder, starting from LSB)




# Mealy → Moore ex 2
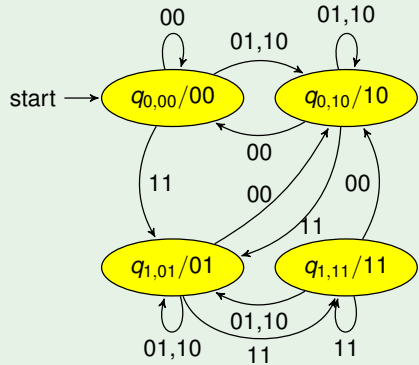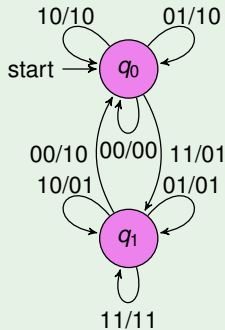
## Example (Serial adder, starting from LSB)



# Mealy → Moore ex 2
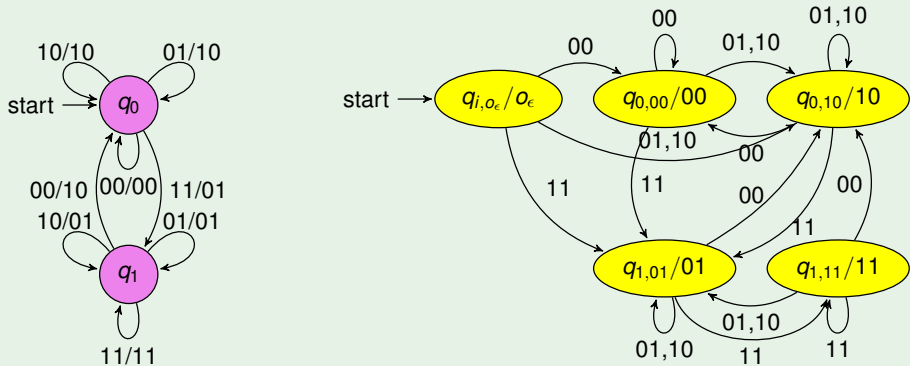
## Example (Serial adder, starting from LSB)




For the adder  $q_{i,o_e}/o_e$  is semantically not needed,  $q_{0,00}/00$  may be retained as the initial state



# Moore→Mealy ex 1

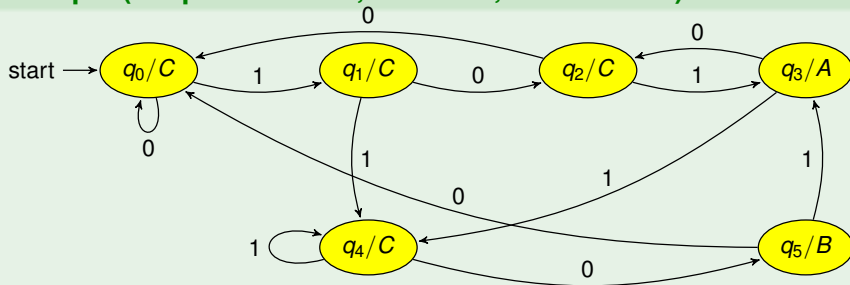Example (Output A on 101, B on 110, C otherwise)



# Moore → Mealy ex 1

Example (Output A on 101, B on 110, C otherwise)

